

CSF Assignment 2 Diagrams


Name: Joon Hyuck Choi

JHED: jchoi100


email: jchoi100@jhu.edu

Problem 1


1. NOR RS Latch

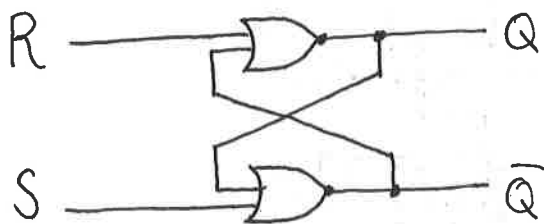

2. D-type Latch

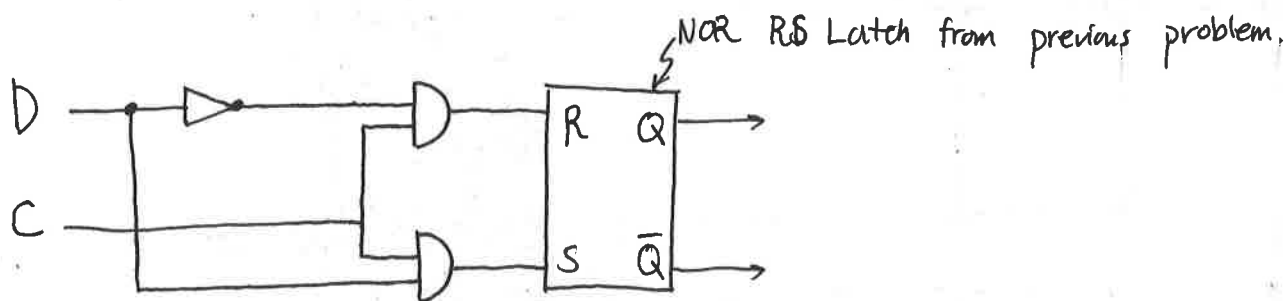


Edge-triggered D-type Flip-flop

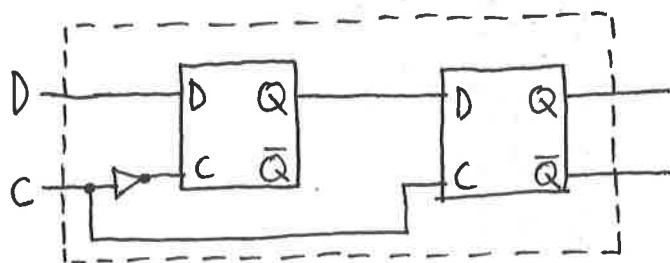


Problem 2. (Please rotate view c.c.w.)

Joon Hyuck Choi
jchoi100@jhu.edu
jchoi100

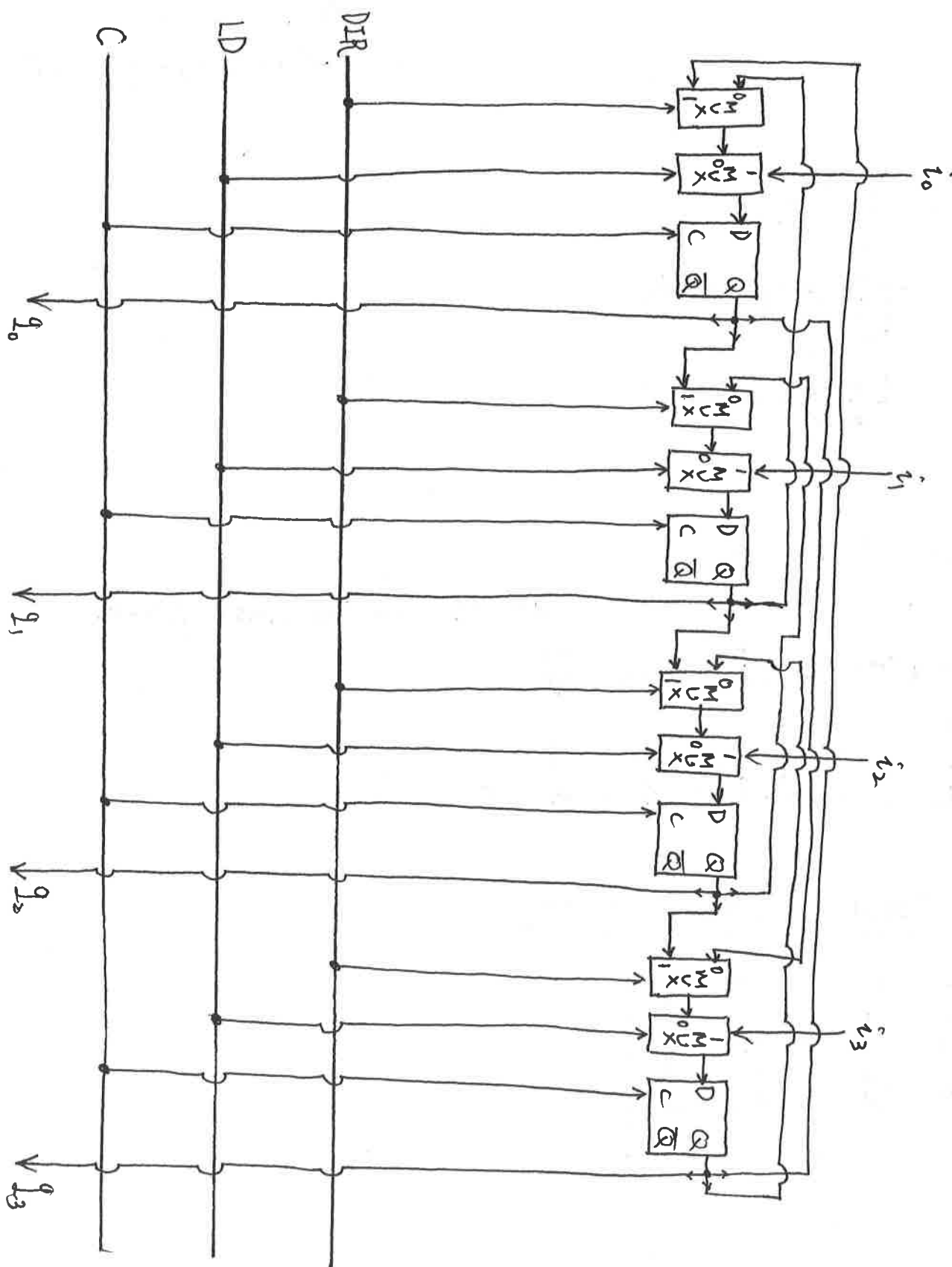

Problem 3.

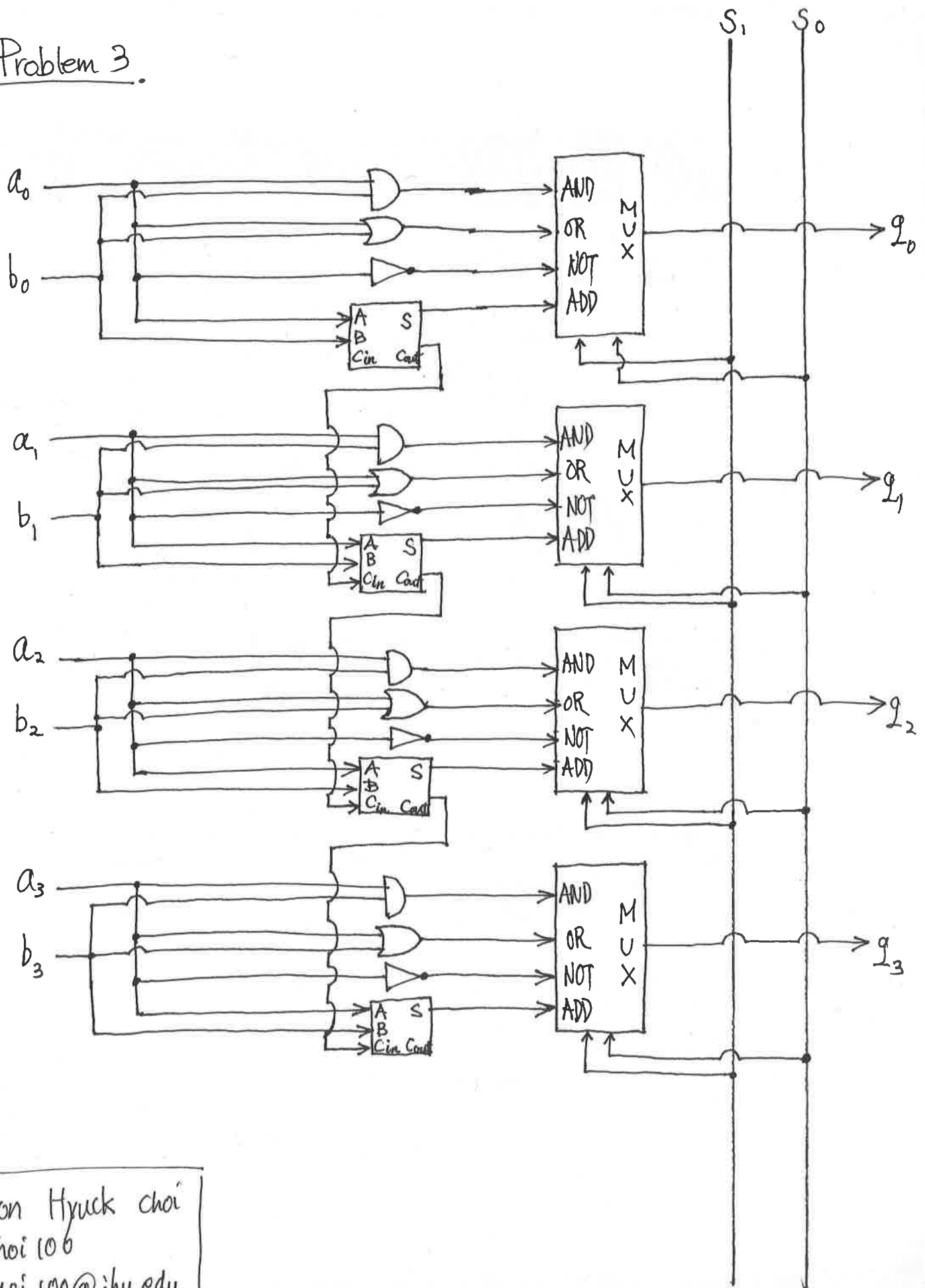

Joon Hyuck Choi
 jchoi106
 jchoi100@jhu.edu